

Hardware Assignment - Report

AI1110: Probability and Random Variables

Indian Institute of Technology Hyderabad

Bonthu Mani Hemanth Reddy

CS22BTECH11013

18 May 2023

Random number generation using Shift Registers

COMPONENTS

Component	Value	Quantity
Breadboard		1
Seven Segment Display	Common Anode	1
Decoder	7447	1
Flip Flop	7474	2
X-OR Gate	7486	1
555 IC		1
Resistor	1 K Ω	1
Capacitor	100 nF	1
Capacitor	10 nF	1
Jumper Wires		

PROCEDURE

- 1) The CLOCK signal is generated using the 555 timer circuit according to the figure 1.

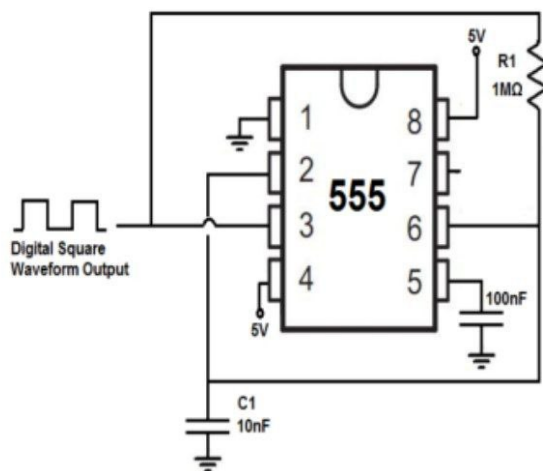


Fig. 1. 555 timer circuit diagram

- 2) The CLOCK output obtained from 555 timer is connected to the clock signal of D-Flip flops that is to each 7474IC.
- 3) Each 7474IC contains 2 D-Flip flop gates. These are used to build a circuit for shift registers. D_i and Q_i refers to the input and output of i^{th} D-Flip flop gate respectively. Output of each D-Flip flop gate acts input for the next D-Flip flop gate i.e. Q_i is connected to D_{i+1}
- 4) The XOR gate (7486 IC) is connected to Q_0, Q_3 for input at 1st, 2nd position and D_0 as output at 3rd position.
- 5) The decoder's (7447 IC) positions labelled as A,B,C,D is connected with output of each D-Flip flop gate that is Q_0, Q_1, Q_2, Q_3 respectively as shown in figure 2.



Fig. 2. Connection in Decoder gate

- 6) Now, the seven segmented display is connected to the the decoder (7447 IC) according to the table 3.
- 7) The Position labelled as COM in seven segmented display is connected to VCC (higher voltage) . Similarly, 7474 IC and XOR gate (7486 IC) is connected to VCC using position labelled as 14th while grounded at 7th position

7447	\bar{a}	\bar{b}	\bar{c}	\bar{d}	\bar{e}	\bar{f}	\bar{g}
Display	a	b	c	d	e	f	g

Fig. 3. Connection of seven segmented display with decoder

. The decoder (7447 IC) is connected to power source and ground at 16th and 8th position respectively .

OUTPUT

The seven-segmented display displays random Integers as displayed in 4, 5 and 6.

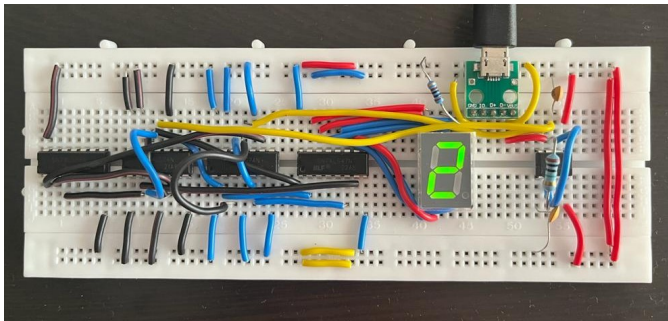


Fig. 4. Image 1 of seven segment display showing number

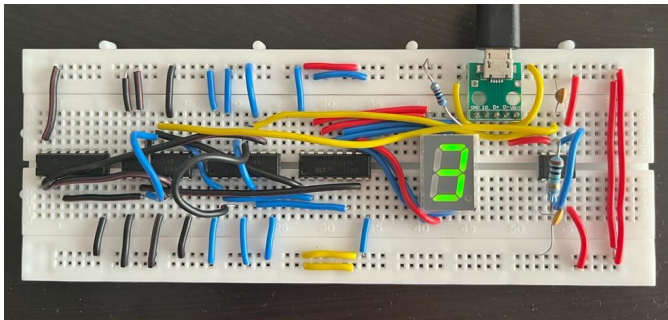


Fig. 5. Image 2 of seven segment display showing number

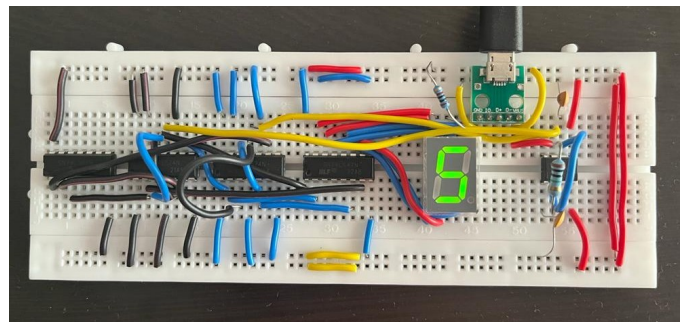


Fig. 6. Image 3 of seven segment display showing number